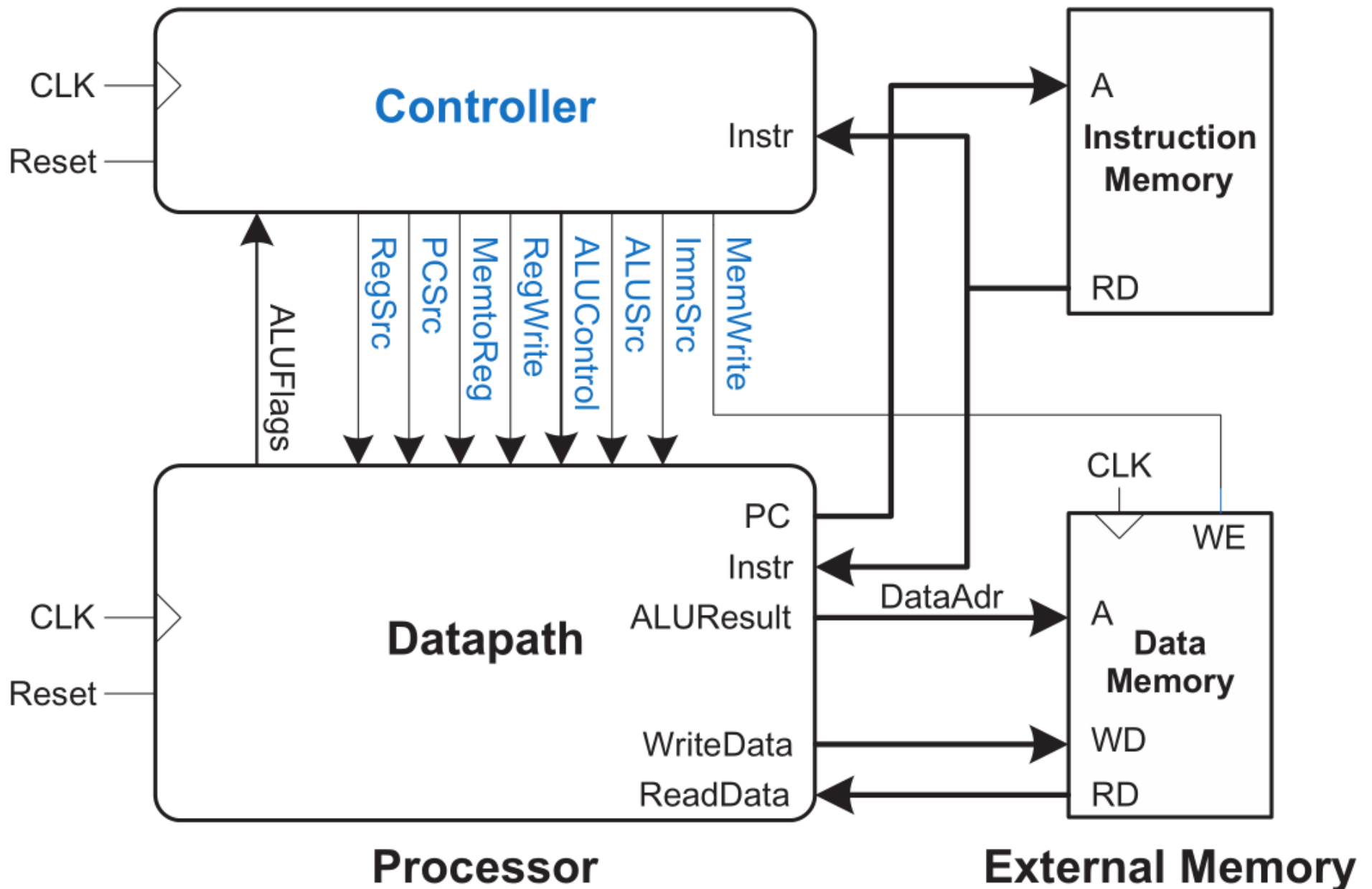


# Computer organization and architecture

## Lesson 17

HDL for the single-cycle processor

# Single-cycle processor



# Single-cycle processor

```
module arm (input          clk, reset,
            input [31:0]   Instr, ReadData,
            output         MemWrite,
            output [31:0]  ALUResult, WriteData, PC);

    wire      RegWrite, ALUSrc, MemtoReg, PCSrc;
    wire [1:0] RegSrc, ImmSrc, ALUControl;
    wire [3:0] ALUFlags;


    controller c(clk, reset, ALUFlags, Instr[31:12], RegSrc,
                 ImmSrc, ALUControl, RegWrite, ALUSrc,
MemWrite,
                 MemtoReg, PCSrc);

    datapath dp(clk, reset, RegWrite, ALUSrc, MemtoReg, PCSrc,
                RegSrc, ImmSrc, ALUControl, Instr, ReadData,
                ALUFlags, PC, ALUResult, WriteData);
endmodule
```

# Top-level module

```
module top(input clk, reset,
           output [31:0] WriteData, DataAdr, Instr,
           output MemWrite);
  wire [31:0] PC, ReadData;
  // instantiate processor and memories
  arm arm(clk, reset, Instr, ReadData, MemWrite,
          DataAdr, WriteData, PC);
  imem imem(PC, Instr);
  dmem dmem(clk, MemWrite, DataAdr, WriteData, ReadData);
endmodule
```

# Controller

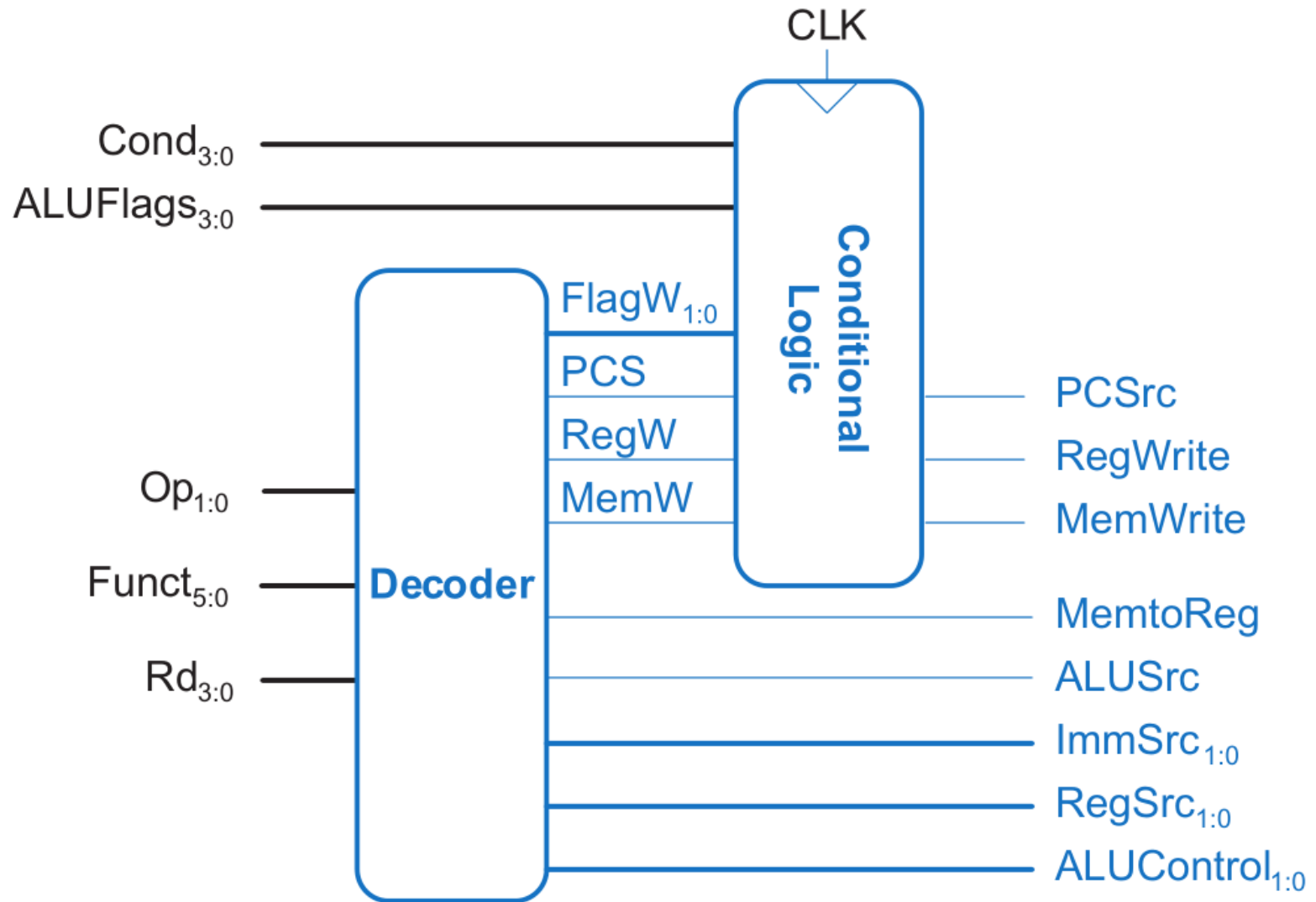

# Controller


```
module controller(input      clk, reset,
                  input [3:0] ALUFlags,
                  input [31:12] Instr,
                  output [1:0] RegSrc, ImmSrc, ALUControl,
                  output      RegWrite, ALUSrc, MemWrite,
                              MemtoReg, PCSrc);

  wire [1:0] FlagW;
  wire PCS, RegW, MemW;

  decoder dec(Instr[27:26], Instr[25:20], Instr[15:12],
             PCS, RegW, MemW, MemtoReg, ALUSrc, FlagW,
             ImmSrc, RegSrc, ALUControl);

  condlogic cl(clk, reset, PCS, RegW, MemW,
              Instr[31:28], ALUFlags, FlagW,
              PCSrc, RegWrite, MemWrite);
endmodule
```

# Decoder

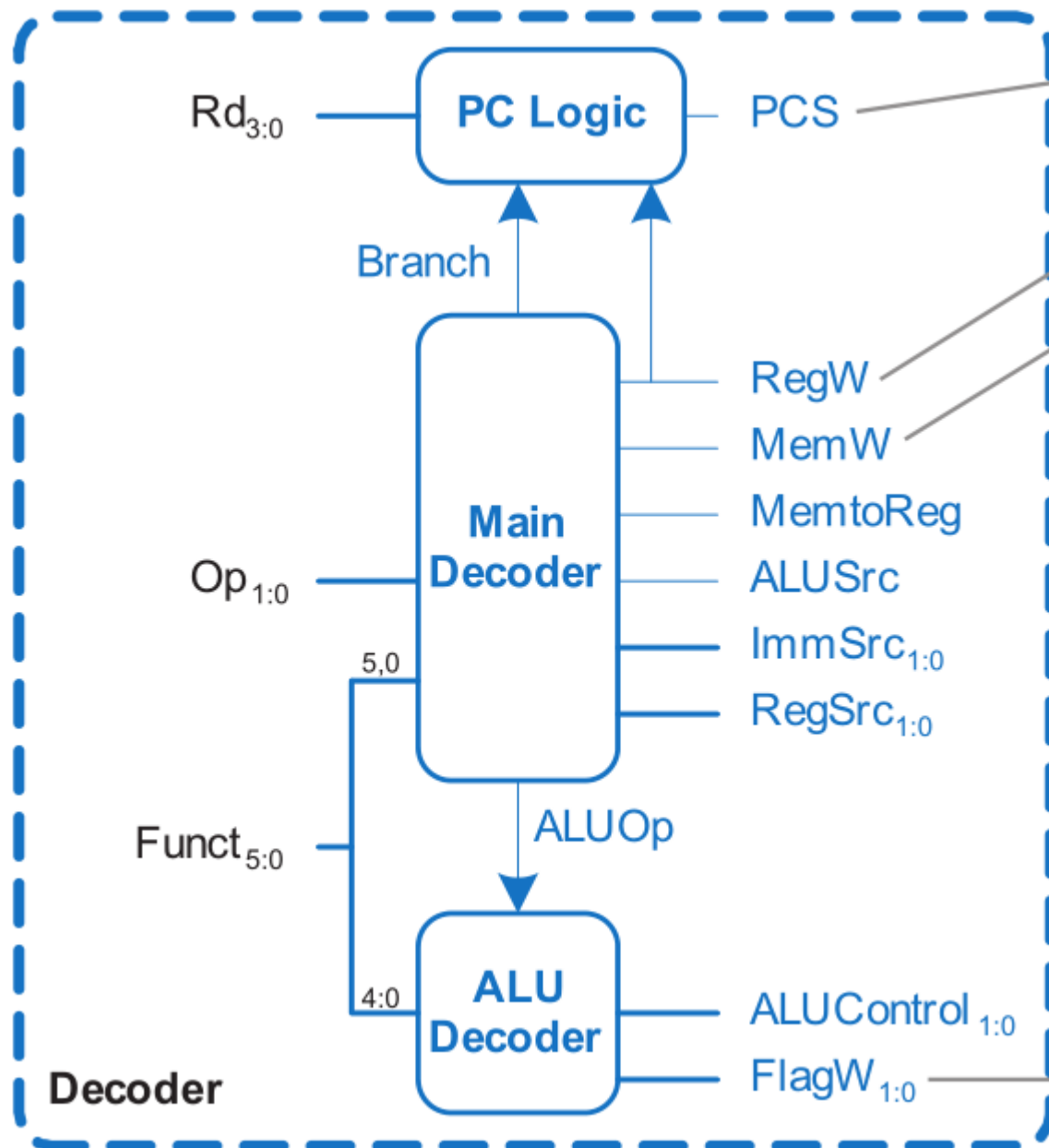

# Decoder

```
module decoder(input [1:0] Op,  
               input [5:0] Funct,  
               input [3:0] Rd,  
               output PCS, RegW, MemW, MemtoReg,  
                  ALUSrc,  
               output [1:0] FlagW, ImmSrc, RegSrc,  
                  ALUControl);  
  
wire Branch, ALUOp;  
  
maindecoder mdec(Op, Funct[5], Funct[0], RegSrc,  
                ImmSrc, ALUSrc, MemtoReg, MemW, RegW,  
                Branch, ALUOp);  
  
ALUdecoder aludec(ALUOp, Funct[4:0], FlagW, ALUControl);  
  
PClogic pcl(Rd, Branch, RegW, PCS);  
  
endmodule
```



# Main decoder

```
module maindecoder(input [1:0] Op,
                   input      Funct5, Funct0,
                   output [1:0] RegSrc, ImmSrc,
                   output      ALUSrc, MemtoReg, MemW, RegW,
                           Branch, ALUOp);

    reg [9:0] controls;

    always @ (*)
        casex(Op)
            2'b00: if (Funct5) controls = 10'b0001001001; // DP imm
                   else        controls = 10'b0000001001; // DP reg
            2'b01: if (Funct0) controls = 10'b0101011000; // LDR
                   else        controls = 10'b0011010100; // STR
            2'b10:        controls = 10'b1001100010; // B
            default:      controls = 10'bx; // Unimplemented
        endcase

    assign {Branch, MemtoReg, MemW, ALUSrc, ImmSrc,
            RegW, RegSrc, ALUOp} = controls;
endmodule
```

# Main decoder

Op	Funct <sub>5</sub>	Funct <sub>0</sub>	Type	Branch	MemtoReg	MemW	ALUSrc	ImmSrc	RegW	RegSrc	ALUOp
00	0	X	DP Reg	0	0	0	0	XX	1	00	1
00	1	X	DP Imm	0	0	0	1	00	1	X0	1
01	X	0	STR	0	X	1	1	01	0	10	0
01	X	1	LDR	0	1	0	1	01	1	X0	0
10	X	X	B	1	0	0	1	10	0	X1	0

```

always @ (*)
  casex(Op)
    2'b00: if (Funct5) controls = 10'b0001001001; // DP imm
           else           controls = 10'b0000001001; // DP reg
    2'b01: if (Funct0) controls = 10'b0101011000; // LDR
           else           controls = 10'b0011010100; // STR
    2'b10:           controls = 10'b1001100010; // B
    default:          controls = 10'bx; // Unimplemented
  endcase

assign {Branch, MemtoReg, MemW, ALUSrc, ImmSrc,
        RegW, RegSrc, ALUOp} = controls;

```

# ALUDecoder

<i>ALUOp</i>	<i>Funct</i> <sub>4:1</sub> ( <i>cmd</i> )	<i>Funct</i> <sub>0</sub> ( <i>S</i> )	Type	<i>ALUControl</i> <sub>1:0</sub>	<i>FlagW</i> <sub>1:0</sub>
0	X	X	Not DP	00 (Add)	00
1	0100	0	ADD	00 (Add)	00
		1			11
	0010	0	SUB	01 (Sub)	00
		1			11
	0000	0	AND	10 (And)	00
		1			10
	1100	0	ORR	11 (Or)	00
		1			10

# ALUDecoder

```
module ALUdecoder(input          ALUOp,
                  input [4:0]    Funct,
                  output reg [1:0] FlagW, ALUControl);


always @ (*)
  if (ALUOp)
    begin // which DP Instr?
      case(Funct[4:1])
        4'b0100: ALUControl = 2'b00; // ADD
        4'b0010: ALUControl = 2'b01; // SUB
        4'b0000: ALUControl = 2'b10; // AND
        4'b1100: ALUControl = 2'b11; // ORR
        default: ALUControl = 2'bx; // unimplemented
      endcase
      FlagW[1] = Funct[0];
      FlagW[0] = Funct[0] &
        (ALUControl == 2'b00 | ALUControl == 2'b01);
    end else begin
      ALUControl = 2'b00; // non-DP instr
      FlagW = 2'b00; // don't update Flags
    end
endmodule
```

# PC Logic

$$PCS = ((Rd == 15) \& RegW) \mid Branch$$

```
module PClogic(input [3:0] Rd,  
               input      Branch, RegW,  
               output      PCS);  
    assign PCS = ((Rd == 4'b1111) & RegW) | Branch;  
endmodule
```

# Conditional Logic

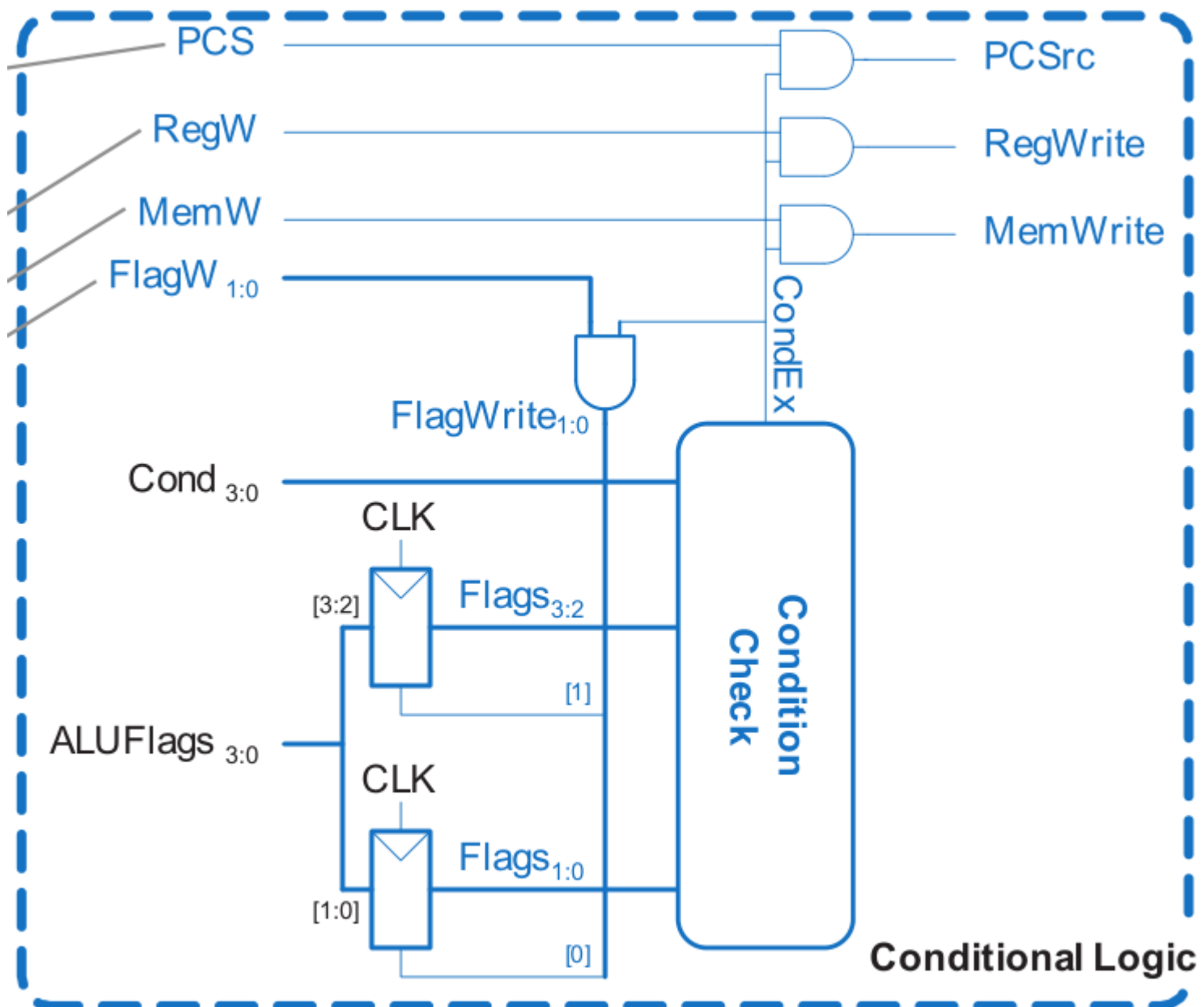

```

module condlogic(input      clk, reset, PCS, RegW, MemW,
                  input [3:0] Cond, ALUFlags,
                  input [1:0] FlagW,
                  output     PCSrc, RegWrite, MemWrite);
wire [1:0] FlagWrite;
wire [3:0] Flags;
wire CondEx;

flopenr #(2)flagreg1(clk, reset, FlagWrite[1],
                    ALUFlags[3:2], Flags[3:2]);
flopenr #(2)flagreg0(clk, reset, FlagWrite[0],
                    ALUFlags[1:0], Flags[1:0]);

condcheck cc(Cond, Flags, CondEx);

assign FlagWrite = FlagW & {2{CondEx}};
assign RegWrite  = RegW  & CondEx;
assign MemWrite  = MemW  & CondEx;
assign PCSrc     = PCS   & CondEx;
endmodule

```

```


module condcheck(input [3:0] Cond, Flags,
                 output reg CondEx);
  wire neg, zero, carry, overflow, ge;
  assign {neg,zero,carry,overflow}=Flags;
  assign ge = (neg == overflow);
  always @ (*)
    case(Cond)
      4'b0000: CondEx = zero; // EQ
      4'b0001: CondEx = ~zero; // NE
      4'b0010: CondEx = carry; // CS
      4'b0011: CondEx = ~carry; // CC
      4'b0100: CondEx = neg; // MI
      4'b0101: CondEx = ~neg; // PL
      4'b0110: CondEx = overflow; // VS
      4'b0111: CondEx = ~overflow; // VC
      4'b1000: CondEx = carry & ~zero; // HI
      4'b1001: CondEx = ~(carry & ~zero); // LS
      4'b1010: CondEx = ge; // GE
      4'b1011: CondEx = ~ge; // LT
      4'b1100: CondEx = ~zero & ge; // GT
      4'b1101: CondEx = ~(~zero & ge); // LE
      4'b1110: CondEx = 1'b1; // Always
      default: CondEx = 1'bx; // undefined
    endcase
endmodule

```

cond	Mnemonic	CondEx
0000	EQ	Z
0001	NE	$\bar{Z}$
0010	CS/HS	C
0011	CC/LO	$\bar{C}$
0100	MI	N
0101	PL	$\bar{N}$
0110	VS	V
0111	VC	$\bar{V}$
1000	HI	$\bar{Z}C$
1001	LS	$Z \text{ OR } \bar{C}$
1010	GE	$\bar{N} \oplus \bar{V}$
1011	LT	$N \oplus V$
1100	GT	$\bar{Z}(\bar{N} \oplus \bar{V})$
1101	LE	$Z \text{ OR } (N \oplus V)$
1110	AL	Ignored



# Datapath

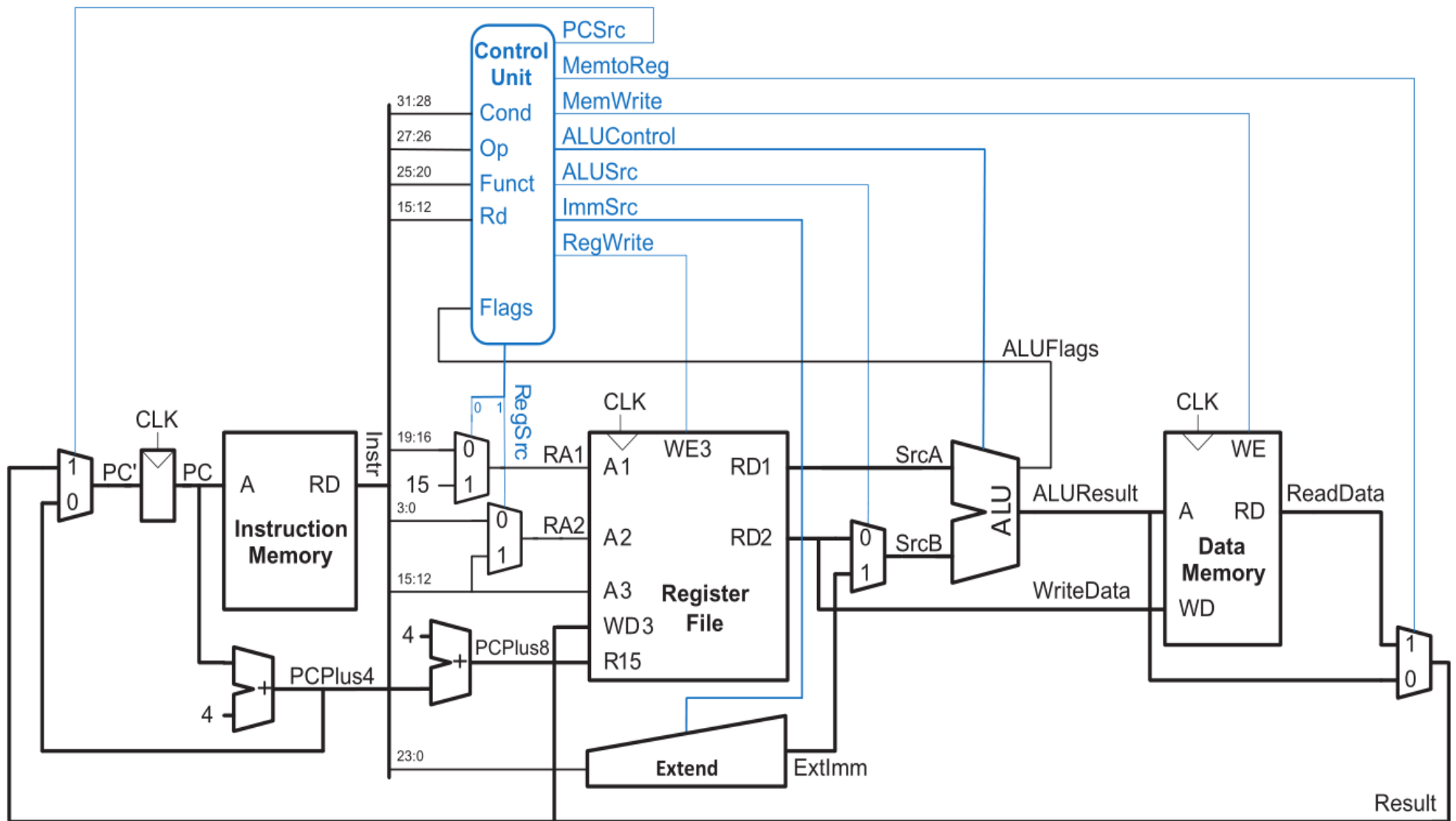

```

module datapath(input clk, reset, RegWrite, ALUSrc, MemtoReg, PCSrc,
                input [1:0]   RegSrc, ImmSrc, ALUControl,
                input  [31:0] Instr, ReadData,
                output [3:0]   ALUFlags,
                output [31:0] PC, ALUResult, WriteData);
wire [31:0] PCNext, PCPlus4, PCPlus8;
wire [31:0] ExtImm, SrcA, SrcB, Result;
wire [3:0] RA1, RA2;
    // next PC logic
mux2 #(32) pcmux(PCPlus4, Result, PCSrc, PCNext);
flopr #(32) pcreg(clk, reset, PCNext, PC);
adder #(32) pcadd1(PC, 32'b100, PCPlus4);
adder #(32) pcadd2(PCPlus4, 32'b100, PCPlus8);
    // register file logic
mux2 #(4) ra1mux(Instr[19:16], 4'b1111, RegSrc[0], RA1);
mux2 #(4) ra2mux(Instr[3:0], Instr[15:12], RegSrc[1], RA2);
regfile rf(clk, RegWrite, RA1, RA2,
            Instr[15:12], Result, PCPlus8, SrcA, WriteData);
mux2 #(32) resmux(ALUResult, ReadData, MemtoReg, Result);
extend ext(Instr[23:0], ImmSrc, ExtImm);
    // ALU logic
mux2 #(32) srcbmux(WriteData, ExtImm, ALUSrc, SrcB);
alu alu(SrcA, SrcB, ALUControl, ALUResult, ALUFlags);
endmodule

```

# ALU

```
module alu(input [31:0] SrcA, SrcB,  
          input [1:0] ALUControl,  
          output [31:0] ALUResult,  
          output [3:0] ALUFlags);  
  wire [31:0] Sum, invSrcB, SignB;  
  wire cout;  
  assign invSrcB = SrcB ^ {32{1'b1}};
```

```
  mux2 #(32) alumux2 (SrcB, invSrcB, ALUControl[0], SignB);  
  addercio #(32) aluadd (SrcA, SignB, ALUControl[0], Sum, cout);  
  mux4 #(32) alumux4 (Sum, Sum, SrcA & SrcB, SrcA | SrcB,  
                    ALUControl, ALUResult);  
  
  assign ALUFlags[3] = ALUResult[31]; // N  
  assign ALUFlags[2] = ~(|ALUResult); // Z  
  assign ALUFlags[1] = ~ALUControl[1] & cout; // C  
  assign ALUFlags[0] = ~ALUControl[1] &  
                      (Sum[31] ^ SrcA[31]) &  
                      ~(ALUControl[0] ^ SrcA[31] ^ SrcB[31]); //V  
  
endmodule
```

<i>ALUControl</i>	Function
-------------------	----------


00	Add
----	-----

01	Subtract
----	----------


10	AND
----	-----

11	OR
----	----

# ALU

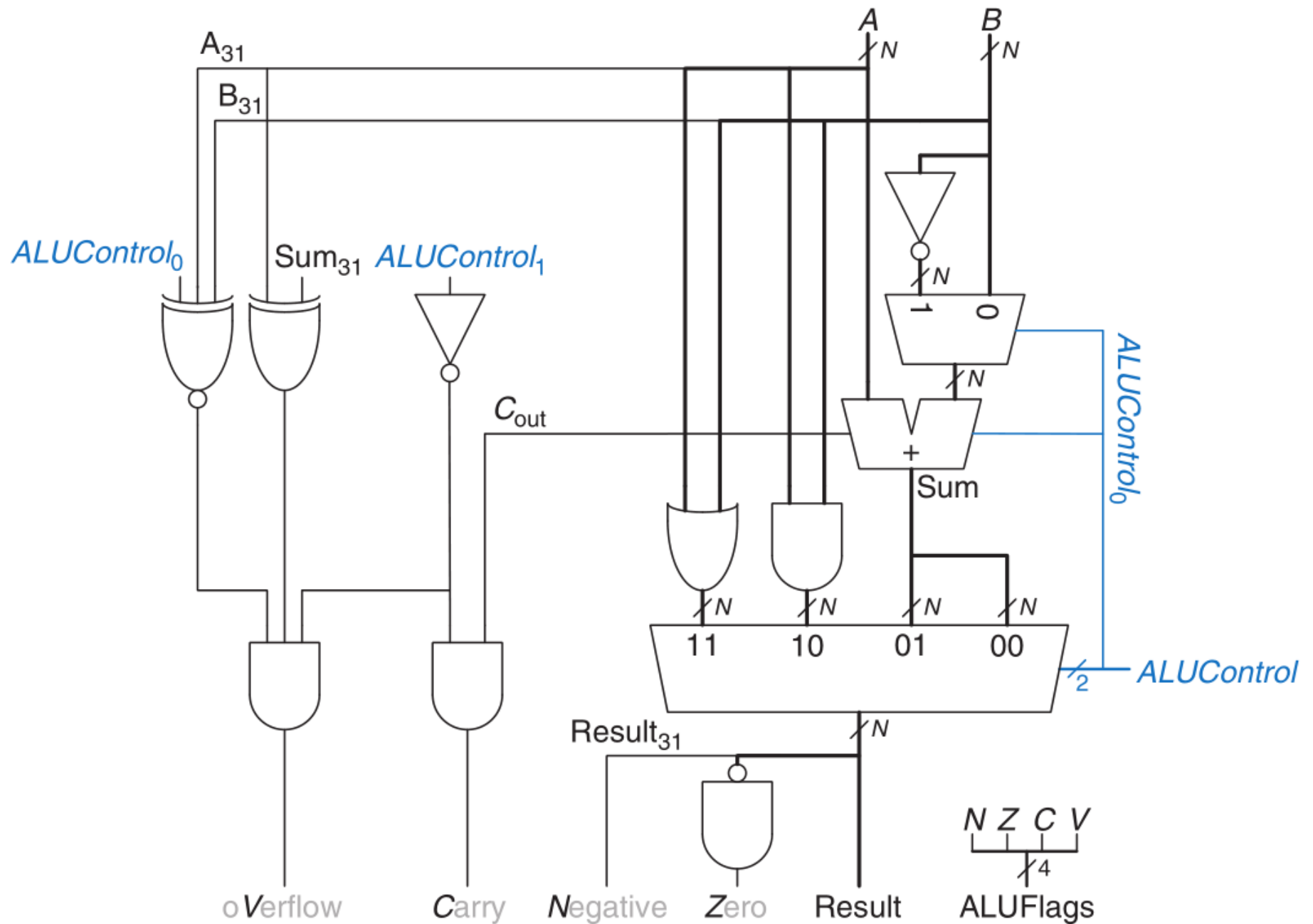

# Register file

 


```
module regfile(input clk, we3,
               input [3:0] ra1, ra2, wa3,
               input [31:0] wd3, r15,
               output [31:0] rd1, rd2);
  reg [31:0] rf[14:0];

  always @(posedge clk)
    if (we3) rf[wa3] <= wd3;

  assign rd1 = (ra1 == 4'b1111) ? r15 : rf[ra1];
  assign rd2 = (ra2 == 4'b1111) ? r15 : rf[ra2];
endmodule
```

 
# Adder

```
module adder #(parameter WIDTH=8)
    (input [WIDTH-1:0] a, b,
     output [WIDTH-1:0] y);
    assign y = a + b;
endmodule
```


 
## Adder with carry in and carry out

```
module addercio #(parameter WIDTH=8)
    (input [WIDTH-1:0] a, b,
     input cin,
     output [WIDTH-1:0] s,
     output cout);
    assign {cout, s} = a + b + cin;
endmodule
```



# Immediate extension

ImmSrc	ExtImm	Description
00	{24 0s} $Instr_{7:0}$	8-bit unsigned immediate for data-processing
01	{20 0s} $Instr_{11:0}$	12-bit unsigned immediate for LDR/STR
10	{6 $Instr_{23}$ } $Instr_{23:0}$ 00	24-bit signed immediate multiplied by 4 for B

```
module extend(input [23:0]      Instr,
              input [1:0]      ImmSrc,
              output reg [31:0] ExtImm);
  always @ (*)
    case(ImmSrc)
      2'b00: ExtImm = {24'b0, Instr[7:0]}; // 8-bit unsigned
      2'b01: ExtImm = {20'b0, Instr[11:0]}; // 12-bit unsigned
      // 24-bit signed
      2'b10: ExtImm = {{6{Instr[23]}}, Instr[23:0], 2'b00};
      default: ExtImm = 32'bx; // undefined
    endcase
endmodule
```

## Resettable flip-flop

```
module flopr #(parameter WIDTH = 8)
    (input clk, reset,
     input [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);
    always @(posedge clk, posedge reset)
        if (reset) q <= {WIDTH{1'b0}};
        else q <= d;
endmodule
```

## Resettable flip-flop with enable

```
module flopenr #(parameter WIDTH = 8)
    (input clk, reset, en,
     input [WIDTH-1:0] d,
     output reg [WIDTH-1:0] q);
    always @(posedge clk, posedge reset)
        if (reset) q <= {WIDTH{1'b0}};
        else if (en) q <= d;
endmodule
```



## 2:1 multiplexer

```
module mux2 #(parameter WIDTH = 8)
    (input [WIDTH-1:0] d0, d1,
     input s,
     output [WIDTH-1:0] y);
    assign y = s ? d1 : d0;
endmodule
```

## 4:1 multiplexer

```
module mux4 #(parameter WIDTH = 8)
    (input [WIDTH-1:0] d0, d1, d2, d3,
     input [1:0] s,
     output [WIDTH-1:0] y);
    assign y = s[1] ? (s[0] ? d3 : d2)
               : (s[0] ? d1 : d0);
endmodule
```

# The testbench loads a program into the memories.

ADDR	PROGRAM	; COMMENTS	HEX CODE
00	MAIN	SUB R0, R15, R15 ; R0 = 0	E04F000F
04		ADD R2, R0, #5 ; R2 = 5	E2802005
08		ADD R3, R0, #12 ; R3 = 12	E280300C
0C		SUB R7, R3, #9 ; R7 = 3	E2437009
10		ORR R4, R7, R2 ; R4 = 3 OR 5 = 7	E1874002
14		AND R5, R3, R4 ; R5 = 12 AND 7 = 4	E0035004
18		ADD R5, R5, R4 ; R5 = 4 + 7 = 11	E0855004
1C		SUBS R8, R5, R7 ; R8 = 11 - 3 = 8, set Flags	E0558007
20		BEQ END ; shouldn't be taken	0A00000C
24		SUBS R8, R3, R4 ; R8 = 12 - 7 = 5	E0538004
28		BGE AROUND ; should be taken	AA000000
2C		ADD R5, R0, #0 ; should be skipped	E2805000
30	AROUND	SUBS R8, R7, R2 ; R8 = 3 - 5 = -2, set Flags	E0578002
34		ADDLT R7, R5, #1 ; R7 = 11 + 1 = 12	B2857001
38		SUB R7, R7, R2 ; R7 = 12 - 5 = 7	E0477002
3C		STR R7, [R3, #84] ; mem[12+84] = 7	E5837054
40		LDR R2, [R0, #96] ; R2 = mem[96] = 7	E5902060
44		ADD R15, R15, R0 ; PC = PC+8 (skips next)	E08FF000
48		ADD R2, R0, #14 ; shouldn't happen	E280200E
4C		B END ; always taken	EA000001
50		ADD R2, R0, #13 ; shouldn't happen	E280200D
54		ADD R2, R0, #10 ; shouldn't happen	E280200A
58	END	STR R2, [R0, #100] ; mem[100] = 7	E5802064

The program in the previous page exercises all of the instructions by performing a computation that should produce the correct result only if all of the instructions are functioning correctly.


The program will write the value 7 to address 100 if it runs correctly, but it is unlikely to do so if the hardware is buggy.

This is an example of **ad hoc testing**.

The machine code is stored in a hexadecimal file called memfile.dat, which is loaded by the testbench during simulation.

The file consists of the machine code for the instructions, one instruction per line.

# Data memory

 


```
module dmem(input clk, we,
            input [31:0] a, wd,
            output [31:0] rd);
    reg [31:0] RAM[63:0];
    assign rd = RAM[a[31:2]]; // word aligned
    always @(posedge clk)
        if (we) RAM[a[31:2]] <= wd;
endmodule
```

```

module imem (input [31:0] adr,
             output reg [31:0] rd);
always @ (adr)
  case (adr)
    32'h00: rd <= 32'hE04F000F;
    32'h04: rd <= 32'hE2802005;
    32'h08: rd <= 32'hE280300C;
    32'h0C: rd <= 32'hE2437009;
    32'h10: rd <= 32'hE1874002;
    32'h14: rd <= 32'hE0035004;
    32'h18: rd <= 32'hE0855004;
    32'h1C: rd <= 32'hE0558007;
    32'h20: rd <= 32'h0A00000C;
    32'h24: rd <= 32'hE0538004;
    32'h28: rd <= 32'hAA000000;
    32'h2C: rd <= 32'hE2805000;
    32'h30: rd <= 32'hE0578002;
    32'h34: rd <= 32'hB2857001;
    32'h38: rd <= 32'hE0477002;
    32'h3C: rd <= 32'hE5837054;
    32'h40: rd <= 32'hE5902060;
    32'h44: rd <= 32'hE08FF000;
    32'h48: rd <= 32'hE280200E;
    32'h4C: rd <= 32'hEA000001;
    32'h50: rd <= 32'hE280200D;
    32'h54: rd <= 32'hE280200A;
    32'h58: rd <= 32'hE5802064;
    32'h5C: rd <= 32'hEAF00000;
  endcase
endmodule

```

# Instruction memory

 

# Testbench

```
module testbench();

    reg clk, reset;
    wire [31:0] WriteData, DataAdr, Instr;
    wire MemWrite;

    // instantiate device to be tested
    top dut(clk, reset, WriteData, DataAdr, Instr, MemWrite);

    initial begin // initialize test
        reset <= 1; #1; reset <= 0;
    end

    always begin // generate clock to sequence tests
        clk = 1; #5; clk = 0; #5;
        if ($time>250) $finish;
    end
    initial
    begin
        $monitor(
            "clk=%b Instr=%h WriteData=%h, DataAdr=%h, MemWrite=%b",
            clk, Instr, WriteData, DataAdr, MemWrite);
    end
endmodule
```

# Good links for learning Verilog

<http://www.verilogpro.com/>

<http://vol.verilog.com/>

<http://www.verilog.com/>

<https://people.ece.cornell.edu/land/courses/ece5760/Verilog/>

<http://www.users.miamioh.edu/jamiespa/verilogTown/index.html>

<https://github.com/verilog-to-routing/vtr-verilog-to-routing>


<https://www.altera.com/support/training/course/ohdl1120.html>

<http://www.asic-world.com/verilog/verilinks.html>


<http://www.ece.uvic.ca/~fayez/courses/ceng465/vlogref.pdf>
 
## Exercise 17.1

In electronic circuits, the contact between two wires is shown as



 The absence of contact (the wires are not connected) is shown as



However, all circuit diagrams in the lessons 14, 15, 16, 17 don't follow this convention (very bad!)

Go through each circuit diagram and mark every contact.

This will be on the quiz and exam.



## Exercise 17.2

Modify the HDL code for the single-cycle ARM processor (in the file `scp.v` in Power Campus) to handle the instructions

CMP

TST

LSL

CMN

ADC

Enhance the testbench to test the new instructions.